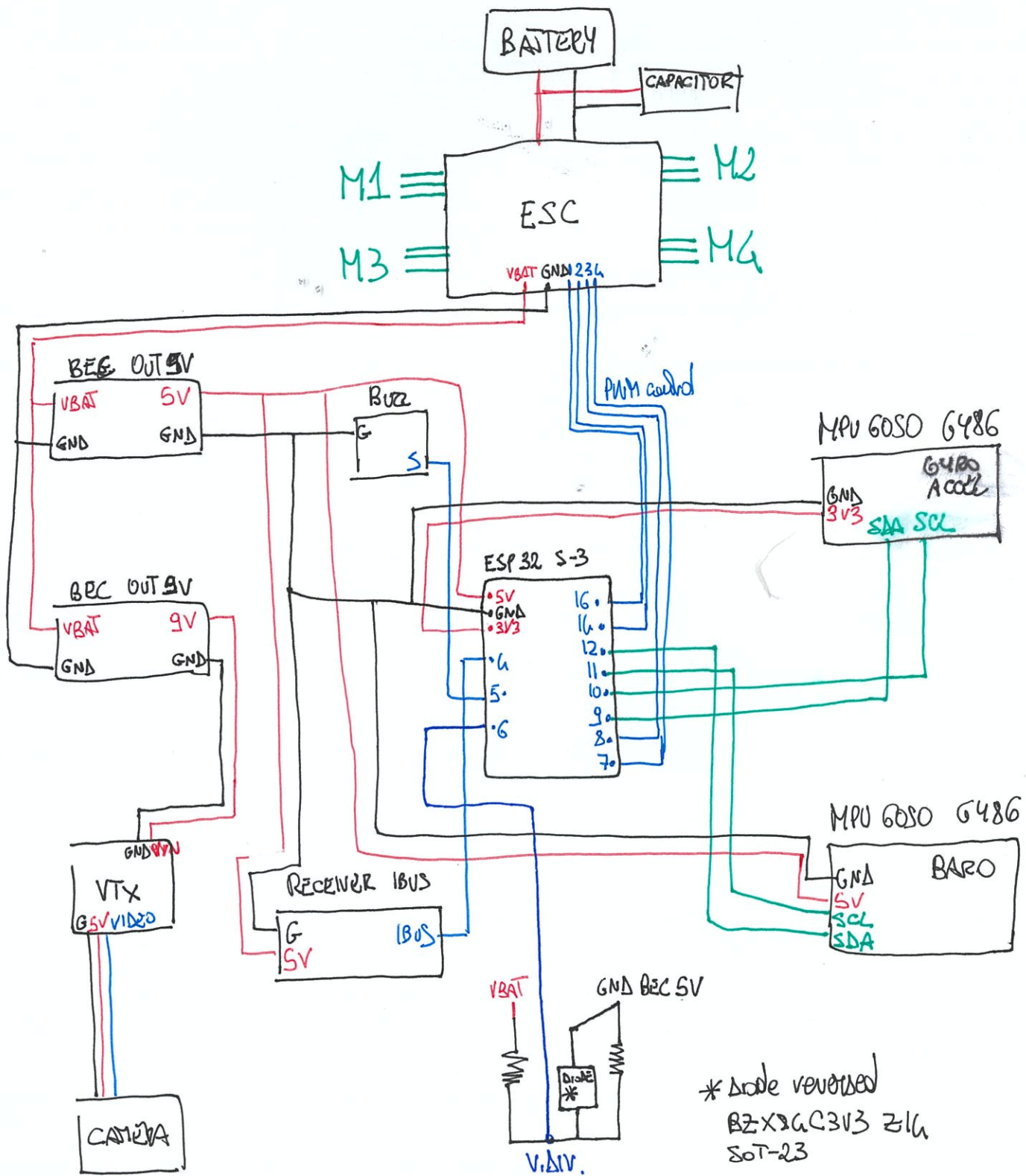




I have 2 BECs in the hope that getting filtered 9V to VTX will improve image quality (next time just place a capacitor)

Resistors I forgot the values, but enough to get 15.17V in and volt. div. at 2.37V.

$R_1 = 5.6k\Omega$
 $R_2 = 0.185k\Omega$
 I do not know the values cause there are also considerations on current not only voltage.